AD5933 Output Impedance

AC coupling at the VOUT output of the AD5933 creates signal attenuation due to the RO/R1/C1 pole and C1/R1 zero. Where RO is the 600Ω output impedance when the AD5933 is configured in output Range 4.

With 1uF and 1.6k Ω C1/R1 combination, the 100 kHz signal is attenuated by approximately 2.8dB.

Changing to the recommended values of 47nF and $25k\Omega$ from the AD5933 datasheet results in a much lower attenuation of approximately 0.2dB.

Equivalent Circuit and Bode plot:



